

WEEK 6 CSE

An automobile alarm circuit used to detect certain undesirable conditions. The three switches are used to indicate the status of the door(D), the ignition(IS), and the headlights(HS), respectively.

Design a logic circuit with these switches as inputs so that the alarm(A) will be activated only when ever either of the following conditions exists:

- The headlights are ON while the ignition is OFF
- The door is open while the ignition is ON

Implement The Above Circuit Using:(1) A 3:8 decoder(74HC238IC) and suitable 2-input logic gates.